


A2: Analog Malicious Hardware

Kaiyuan Yang, Matthew Hicks, Qing Dong, Todd Austin, and Dennis
Sylvester

University of Michigan

A photograph of the Leaning Tower of Pisa, a famous Italian bell tower, leaning to the right. The tower is white with multiple levels of arches. In the background, there are other buildings with red-tiled roofs and a clear blue sky with scattered white clouds. A large crowd of people is gathered at the base of the tower and in the foreground.

Foundations are important

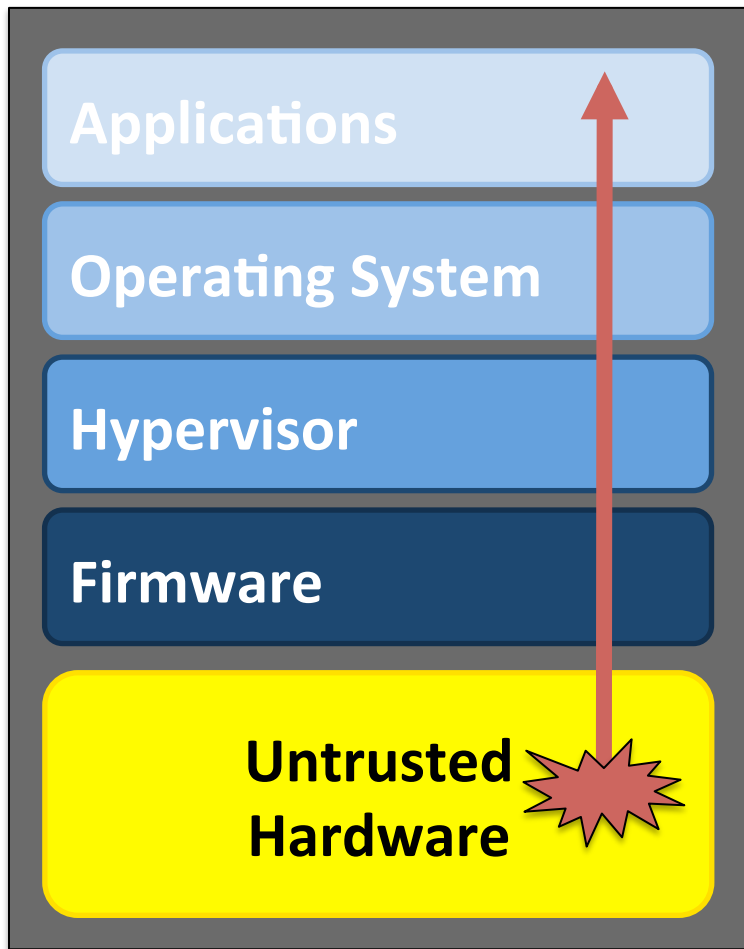

Weakened hardware
weakens the entire
system

Software security success forces attackers to
lower layers



Software security success forces attackers to lower layers




Visual Inspection Side Channels

Dynamic + Static Analysis




catches attacks that are large
because they use additional
logic to hide from dynamic
analysis

catches attacks that are small
because they are always on

 Challenge: construct an attack that is stealthy and small



   Challenge: construct an attack that is stealthy and small



Two threats, we focus on the stage that restricts the attacker the most


Back-end house netlist

```
/*
#####
# Generated by: Cadence Encounter 10.13-s209_1
# OS: Linux x86_64(Host ID vlsipool-
f01.eecs.umich.edu)
# Generated on: Sun May 31 20:06:29 2015
# Design: MAL_TOP
# Command: saveNetlist -excludeLeafCell -lineLength
10000000 -inc...
#####
*/
module arbiter_ibus_slave0_addr_width17_slave1_addr_width28_DW01
_inc_0 (A, SUM, VDD, VSS);
  input [6:0] A;
  output [6:0] SUM;
  inout VDD;
  inout VSS;

  // Internal wires
  wire FE_PHN5383_watchdog_timer_0_;
  wire [6:2] carry;

  // Module instantiations
  DLY4X0P5MA10TR POSCTS FE_PHC5383_watchdog_timer_0_
  (.Y(FE_PHN5383_watchdog_timer_0_
  _), .A(A[0]), .VDD(VDD), .VSS(VSS));
  ADDHX1MA10TR U1_1_5
  (.S(SUM[5]), .CO(carry[6]), .B(carry[5]), .A(A[5]), .VDD(VDD), .V
  SS(VSS));
  ADDHX1MA10TR U1_1_2
  (.S(SUM[2]), .CO(carry[3]), .B(carry[2]), .A(A[2]), .VDD(VDD), .V
  SS(VSS));
  ADDHX1MA10TR U1_1_4
  (.S(SUM[4]), .CO(carry[5]), .B(carry[4]), .A(A[4]), .VDD(VDD), .V
  SS(VSS));
  ADDHX1MA10TR U1_1_3
  (.S(SUM[3]), .CO(carry[4]), .B(carry[3]), .A(A[3]), .VDD(VDD), .V
  SS(VSS));
  ADDHX1MA10TR U1_1_1 (.S(SUM[1]), .CO(carry[2]), .B(FE_PHN5383
  _watchdog_timer_0_), .A(A[1]), .VDD(VDD), .VSS(VSS));
  XOR2X0P7MA10TR U2
  (.Y(SUM[6]), .B(A[6]), .A(carry[6]), .VDD(VDD), .VSS(VSS));
  INVX0P5BA10TR U3 (.Y(SUM[0]), .A(A[0]), .VDD(VDD), .VSS(VSS));
endmodule
```

Foundry GDSII

 


We leverage analog behavior to construct an attack that is stealthy and small

```
on_every(RBACE) do
  if(count == 12345) then
    do_attack()
  else
    count = count + 1
  done
```

RBACE = rare, but attacker controllable event



We leverage analog behavior to construct an attack that is stealthy and small
 
```
on_every(RBACE) do
  if(count == 12345) then
    do_attack()
  else
    count = count + 1
  end
end
```





RBACE = rare, but attacker controllable event



An ideal analog trigger

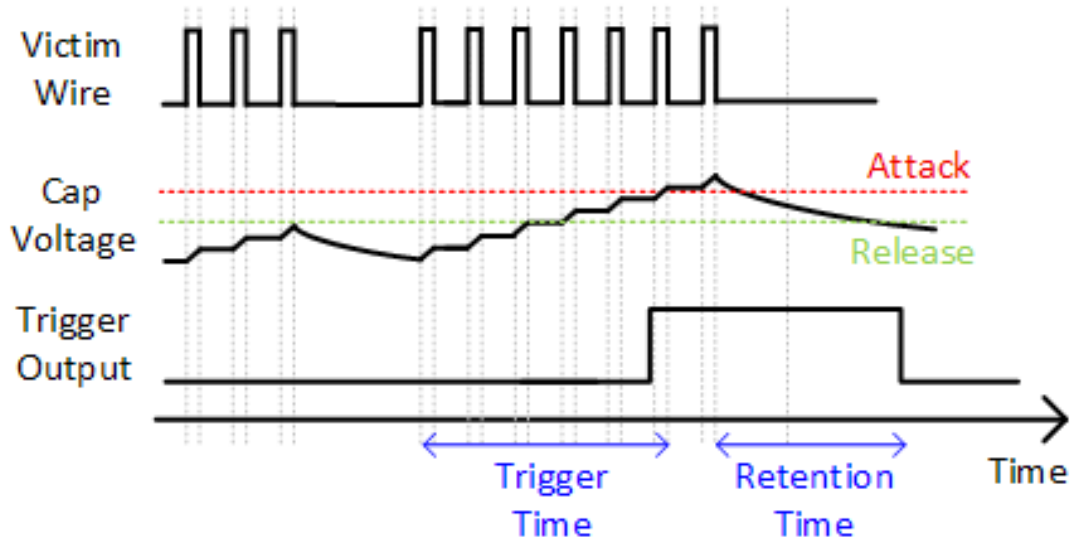 



An ideal analog trigger

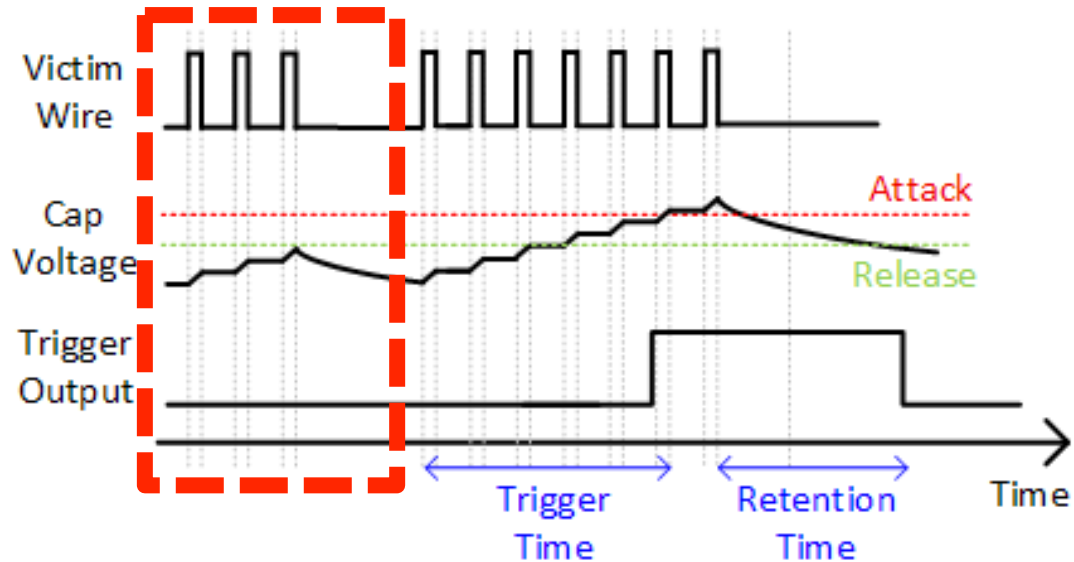 


An ideal analog trigger

  


An ideal analog trigger

  

 
Challenge: small capacitors charge quickly,
large capacitors induce current spikes



 
Challenge: small capacitors charge quickly,
large capacitors induce current spikes




 
Challenge: small capacitors charge quickly,
large capacitors induce current spikes





Solution: charge sharing

 

 
 
Creating an analog trigger using gated charge sharing



  
Creating an analog trigger using gated charge sharing



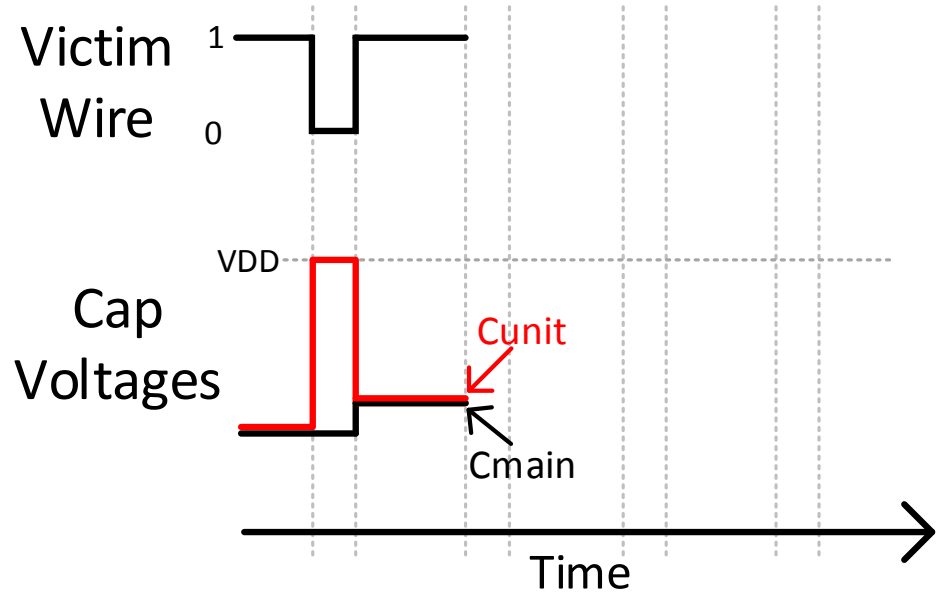 Creating an analog trigger using gated charge sharing




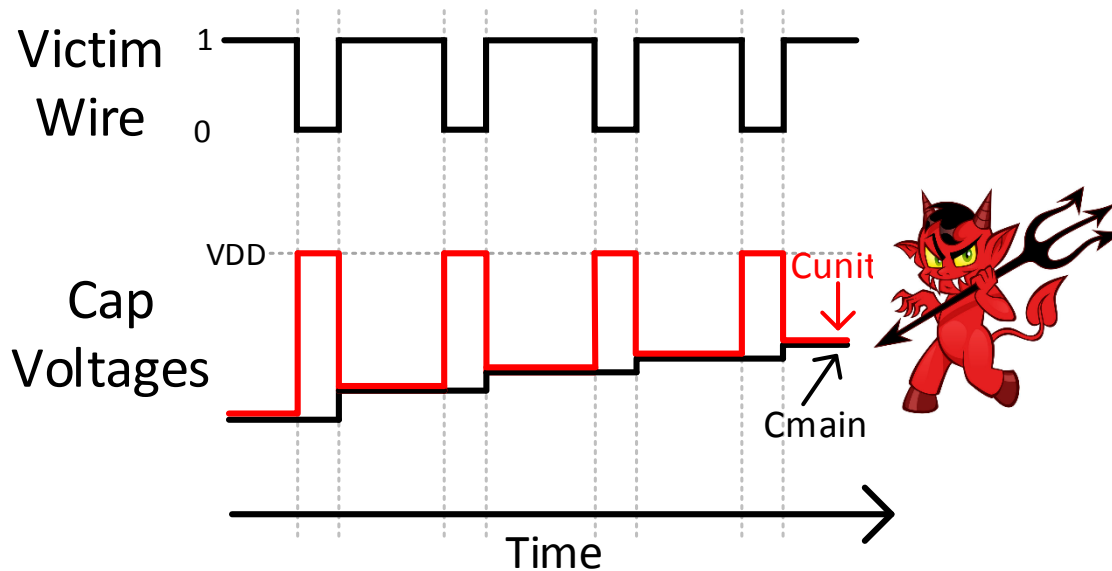Creating an analog trigger using gated charge sharing




Creating a privilege escalation attack

*Our analog trigger is attack agnostic

 


Inverted reset

 


Positive reset

A2

 

 Implanting A2 into an existing chip layout




A2
Trigger

20% to 30%
of chip area
is **unused**



Other challenges in the paper

- Analog circuit design process
- Finding a suitable victim wire
- Finding the flip-flop to attack
- Building multi-stage attacks
- Writing trigger activation code
- Covertly testing for attack success


We had to build A2 to know it worked

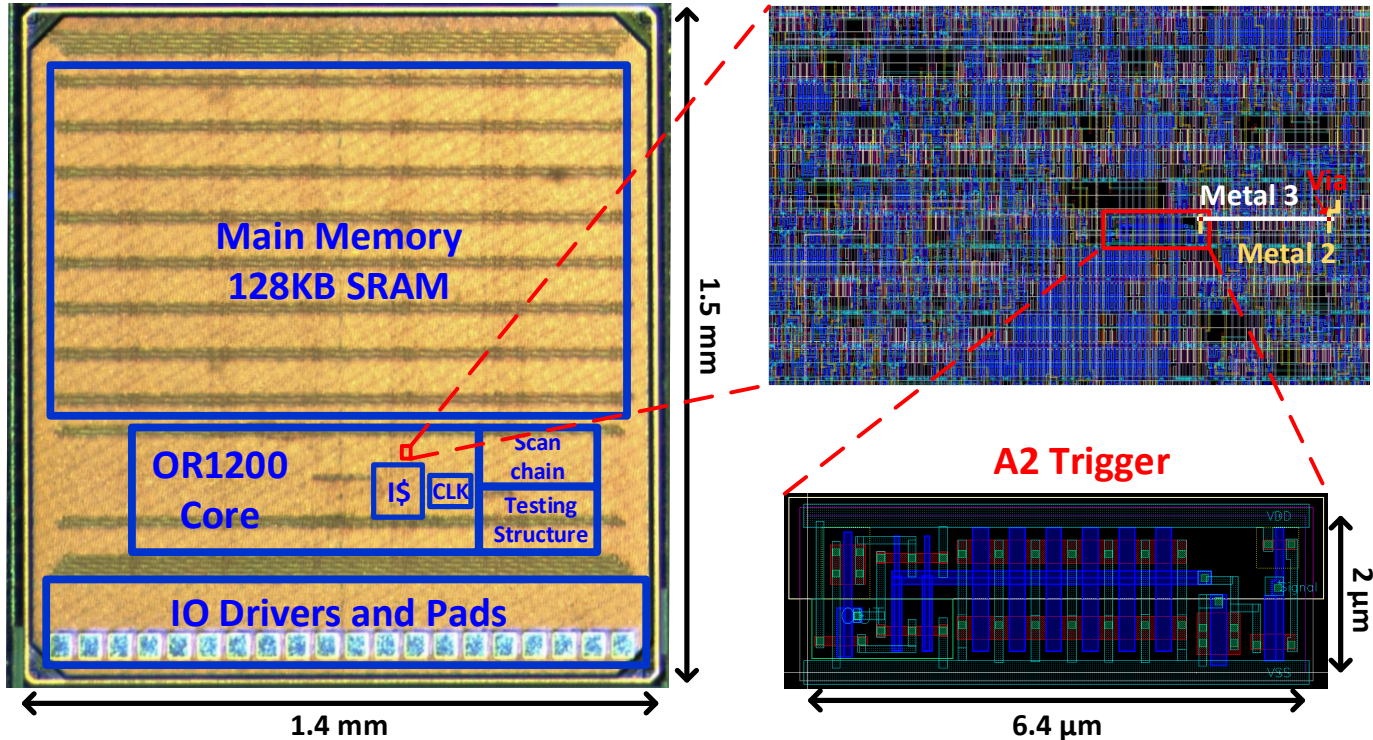

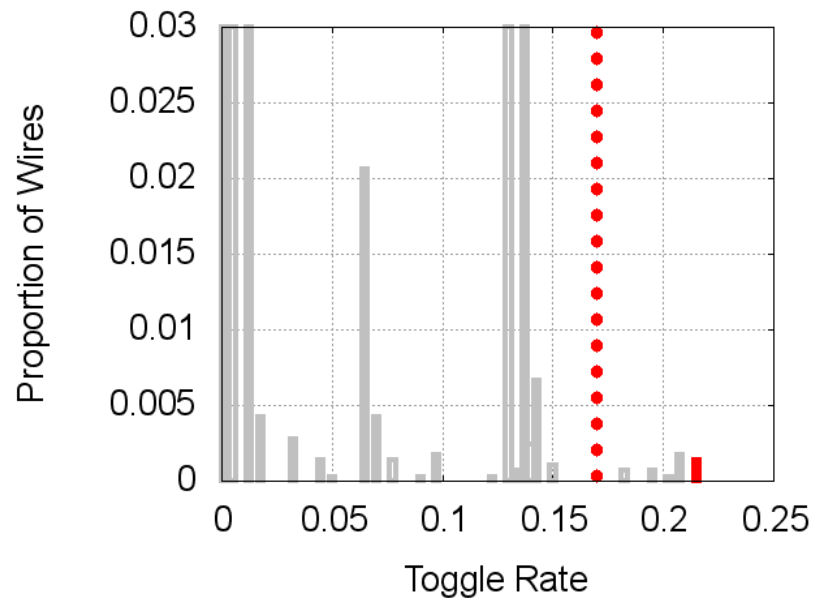 
We activate A2 in real hardware using only user mode code




A2 is hidden from post-fab testing

 

 
Attackers can reliably model their attacks



 Attackers can reliably model their attacks



 Attackers can reliably model their attacks



Attackers can reliably model their attacks

Trigger Circuit	Toggle Rate (MHz)	Measured (10 chip avg)	Simulated (Typical corner)
w/o IO device	120.00	7.4	7
w/o IO device	34.29	8.4	8
w/o IO device	10.91	11.6	10

More experiments in the paper

- Comparison of different standard cell sizes and out attack
- Distribution of trigger times
- Distribution of retention times
- Effect of voltage on cycles to trigger
- Effect of temperature on cycles to trigger
- Effect of temperature on retention time
- Power of benchmarks and attack programs

Cross-domain attacks are stealthy and controllable

- A2 spans the analog and digital domains
- A2 is controllable
- A2 is stealthy
 - complex and unlikely trigger sequence
 - a single cell
- Currently, only detectable post-fabrication

We need to try something
different:

detection
plus
protection



Research artifacts: github.com/impedimentToProgress/A2

Me: [ImpedimentToProgress.com](https://impedimenttoprogress.com)

Fabricator	Popular offshore corp.
Interface	GDSII
Turnaround time	3 months
Added time to project	1 year
Area	1.5mm x 1.5mm
Core	330um x 550um
Memory	1145um x 765um
Process	65nm
Number of chips	100
Cost	\$5k to \$10k per 1mm ²
Other costs	packaging